


Digital Integrated Circuits

A Design Perspective


Chapter 5

Arithmetic Circuits

A Generic Digital Processor

 

Bit-Sliced Datapath

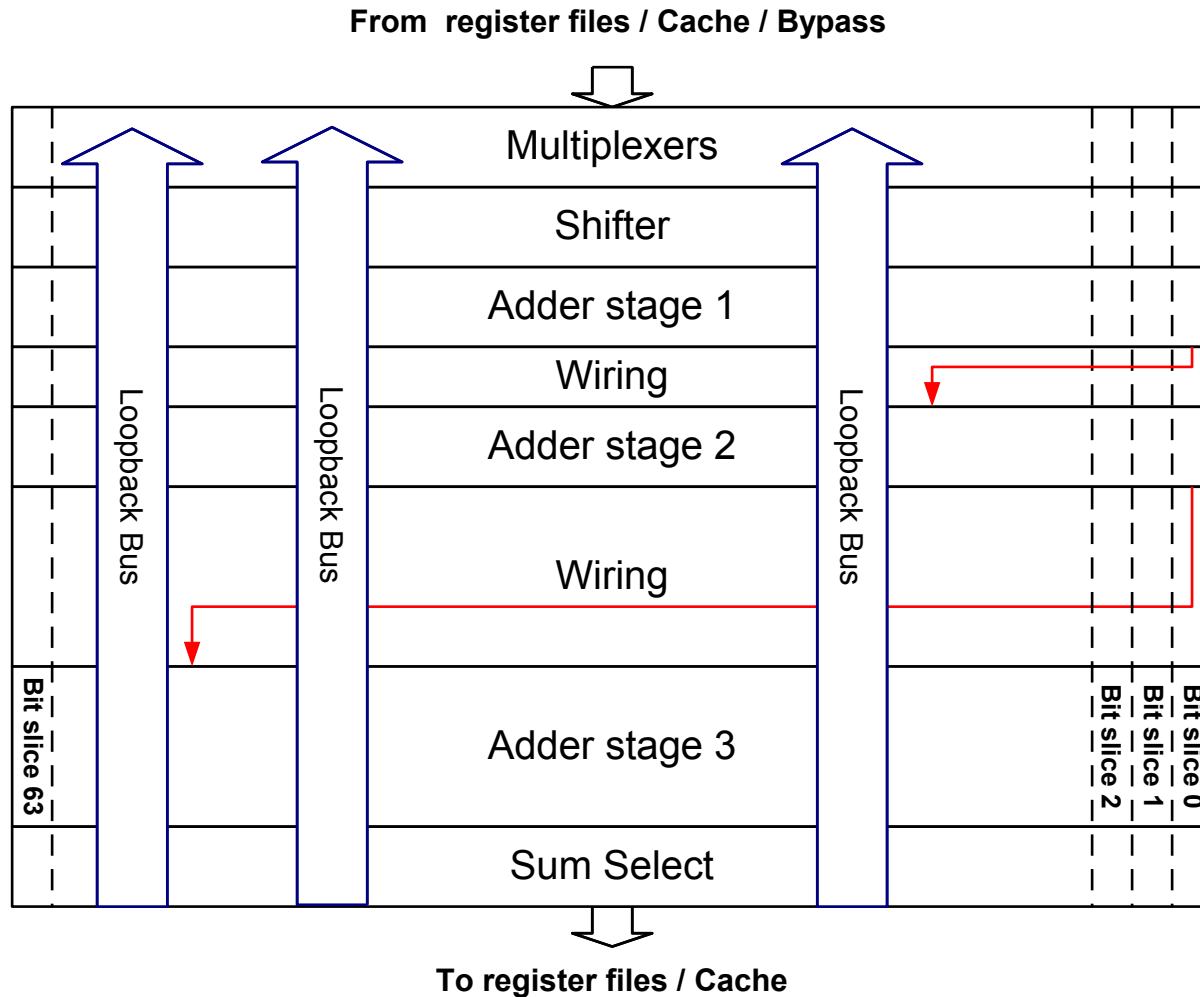

outline

- Adder
- Datapath functional unit
 - Comparators
 - Shifters
 - Multi-input Adders
- Multipliers

Adders

Multitudes of contrivances were designed, and almost endless drawings made, for the purpose of economizing the time and simplifying the mechanism of carriage

—charles babbage, on difference engine No.1, 1864

Outline

- Single-bit Addition
- Carry-Ripple Adder
- Carry-Skip Adder
- Carry-Lookahead Adder
- Carry-Select Adder
- Carry-Increment Adder
- Tree Adder

PGK

- For a full adder, define what happens to carries
 - Generate: $C_{out} = 1$ independent of C
 - $G =$
 - Propagate: $C_{out} = C$
 - $P =$
 - Kill: $C_{out} = 0$ independent of C
 - $K =$

PGK

- For a full adder, define what happens to carries
 - Generate: $C_{out} = 1$ independent of C
 - $G = A \cdot B$
 - Propagate: $C_{out} = C$
 - $P = A \oplus B$
 - Kill: $C_{out} = 0$ independent of C
 - $K = \sim A \cdot \sim B$
- Note that we will be sometimes using an alternate definition for (only for carry)

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$


Propagate (P) = A + B

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = AB$$

 

A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

$$= A \oplus B \oplus C = P \oplus C$$


$$C_{out} = AB + (A + B)C$$

$$= \overline{\overline{A}\overline{B}} + \overline{\overline{A} + \overline{B}}\overline{C} = MAJ(A, B, C)$$

Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 


A	B	C	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = AB$$

 

A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

$$= A \oplus B \oplus C = P \oplus C$$


$$C_{out} = AB + (A + B)C$$

$$= \overline{\overline{A}\overline{B} + (\overline{A} + \overline{B})\overline{C}} = MAJ(A, B, C)$$

Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 

A	B	C	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

delete

propagate



generate

Full Adder Design I

- implementation from eqns

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$


 
 


$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

$$= A \oplus B \oplus C = P \oplus C$$

$$C_{out} = AB + (A + B)C$$
   
$$= \overline{\overline{A}\overline{B}} + (\overline{\overline{A} + \overline{B}})\overline{C} = MAJ(A, B, C)$$



Fewer than mentioned above because of sharing some transistors for XOR gate

Full Adder Design II

- Factor S in terms of C_{out}


$$S = ABC + (A + B + C)(\sim C_{out})$$

$$C_{out} = \text{MAJ}(A, B, C)$$

- Critical path is usually C to C_{out} in ripple adder

$$C_o = AB + BC_i + AC_i$$
 
$$S = ABC_i + \overline{C_o}(A + B + C_i)$$




$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$

$$= A \oplus B \oplus C = P \oplus C$$


$$C_{out} = AB + (A + B)C$$
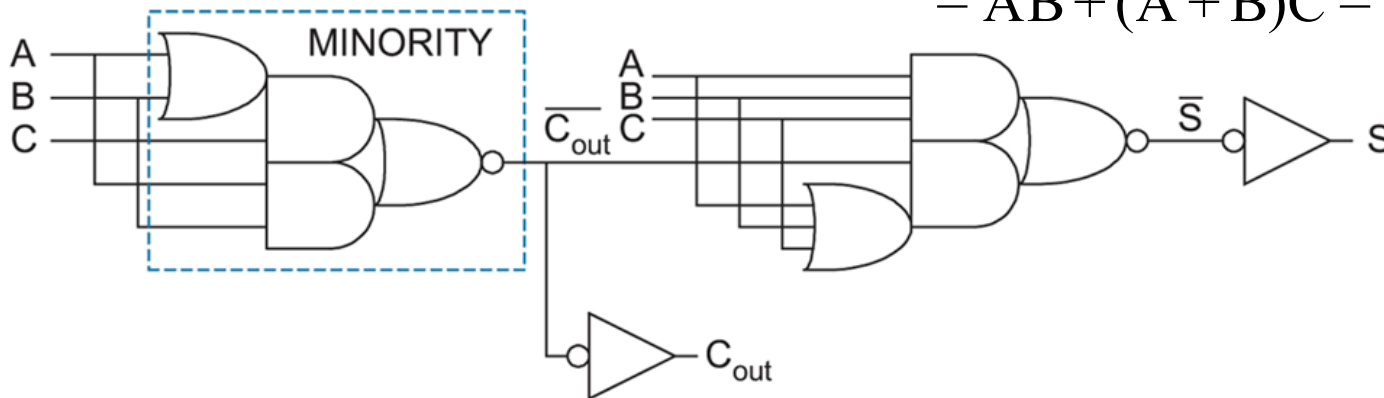
$$= \overline{\overline{A}\overline{B}} + (\overline{A} + \overline{B})\overline{C} = \text{MAJ}(A, B, C)$$



Full Adder Design II

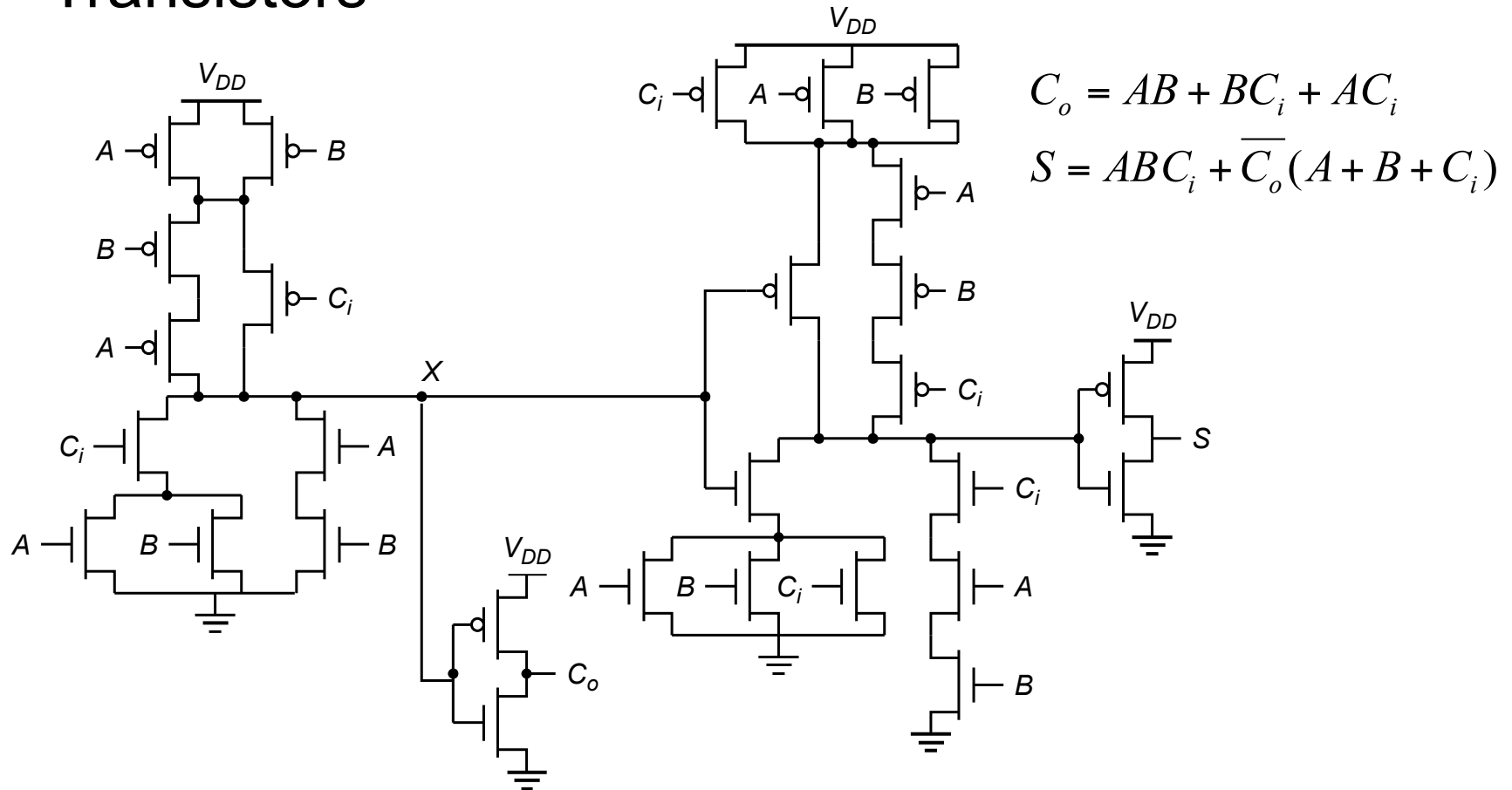
Complimentary Static CMOS Full Adder__28 Transistors



Mirror Adder-Stick Diagram

$$C_o = AB + BC_i + AC_i$$

 
$$S = ABC_i + \overline{C_o}(A + B + C_i)$$



The Mirror Adder

- The NMOS and PMOS chains symmetrical. A maximum of two series transistors arranged in the carry-generation
- the most critical issue is the minimization of the capacitance at node C_o . The reduction of the diffusion capacitances is particularly important.
- The capacitance at node C_o is composed of 4 diffusion capacitances, 2 internal gate capacitances, and 6 gate capacitances in the connecting adder cell .
- The transistors connected to C_i are closest to the output.
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be minimal size.


Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$


 
Minimize Critical Path by Reducing Inverting Stages




Exploit Inversion Property

Transmission Gate


AND

  



Mux

 

Pass-Transistor Based

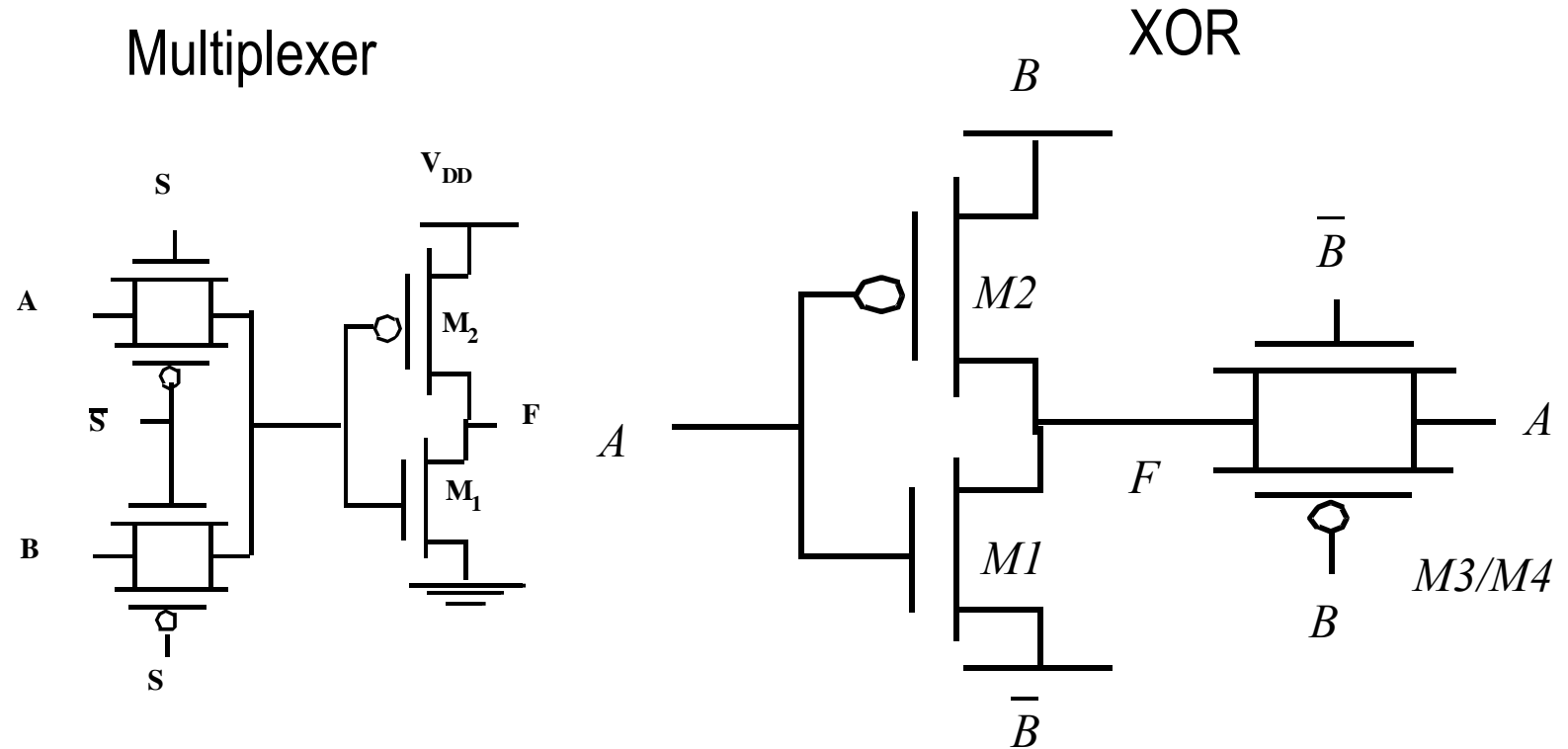


Complementary Pass Transistor Logic

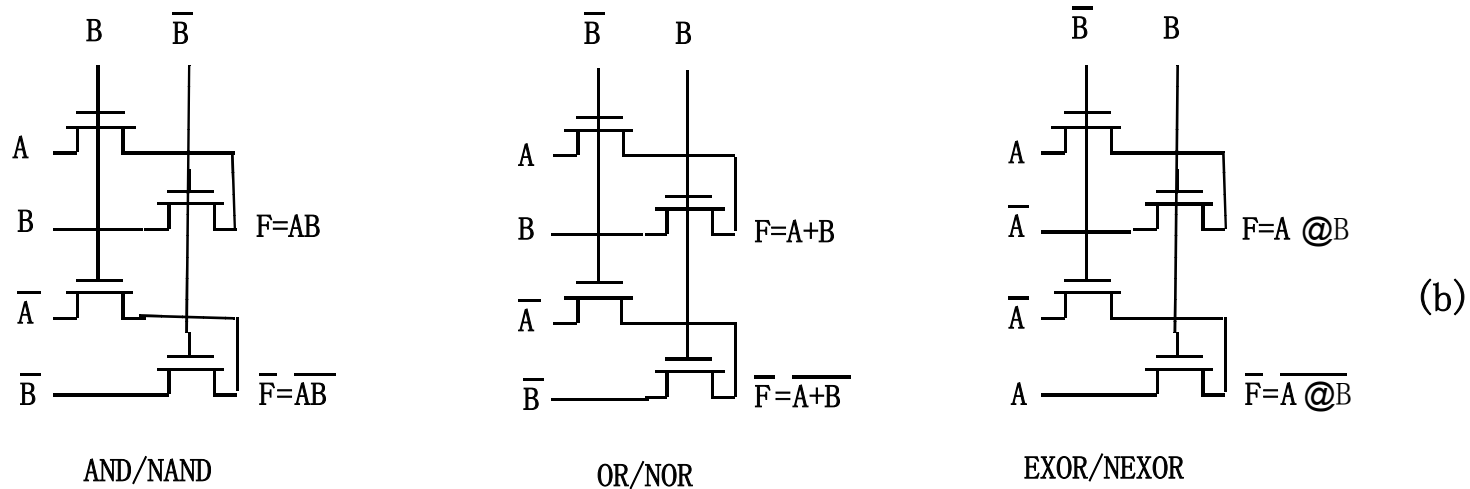 

Full Adder Design III

 - Complementary Pass Transistor Logic (CPL)
 - Slightly faster, but more area



Full Adder Design IV



A⊕B

$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$


$$= A \oplus B \oplus C = P \oplus C$$

$$C_{out} = AB + (A \oplus B)C = AAB + \overline{A}\overline{A}\overline{B} + (A \oplus B)C$$
  
$$= A(\overline{A \oplus B}) + (A \oplus B)C$$



Manchester Carry Chain

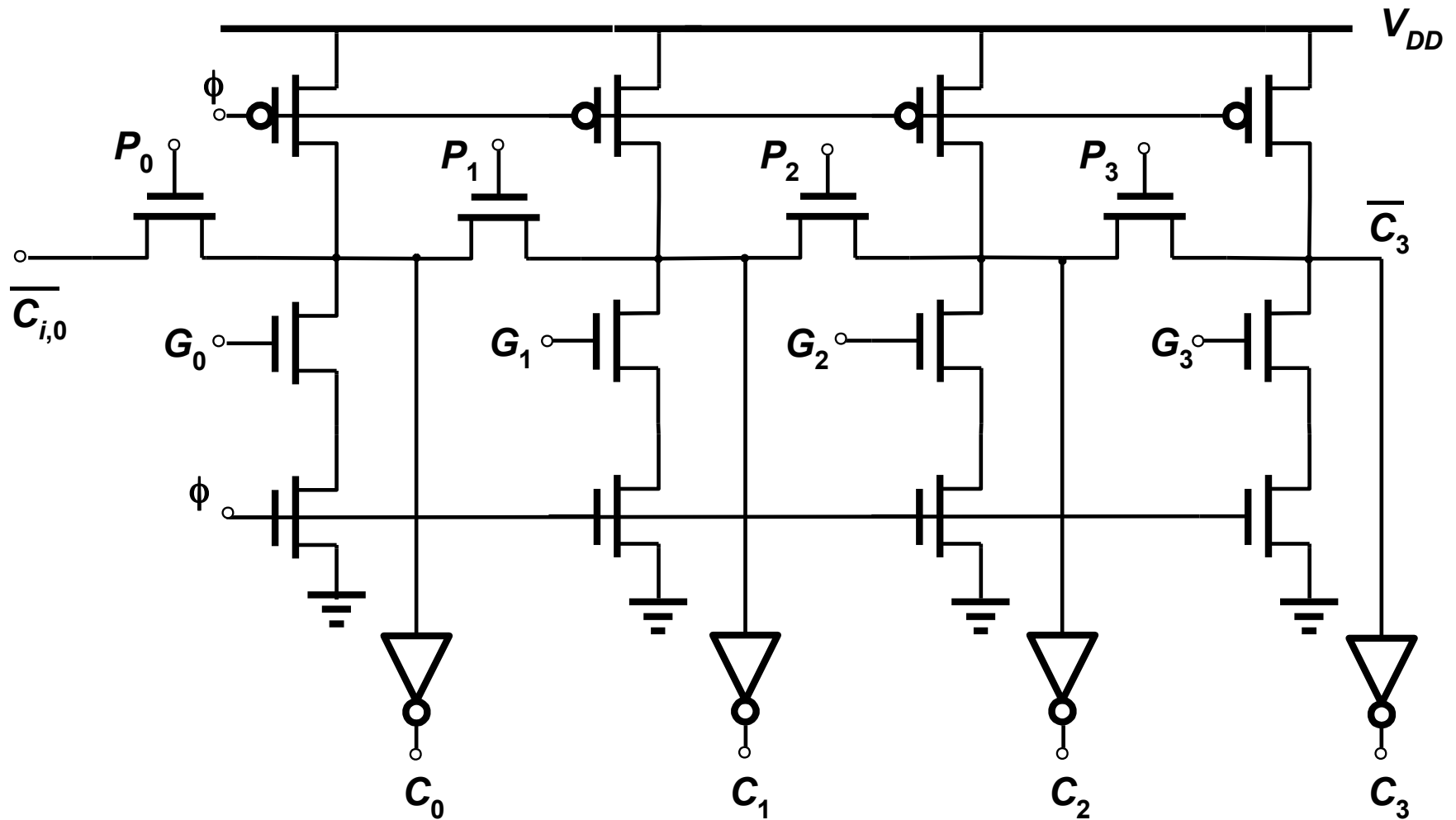

Generate / Propagate

- Equations often factored into G and P
- Generate and propagate for groups spanning i:j

$$G_{i:j} = G_{i:k} + P_{i:k} g G_{k-1:j}$$

- Base case $P_{i:j} = P_{i:k} g P_{k-1:j}$


$$G_{i:i} \equiv G_i = A_i g B_i$$

$$G_{0:0} \equiv G_0 = C_{in}$$

- Sum: $P_{i:i} \equiv P_i = A_i \oplus B_i$ $P_{0:0} \equiv P_0 = 0$

$$S_i = P_i \oplus G_{i-1:0}$$

PG Logic

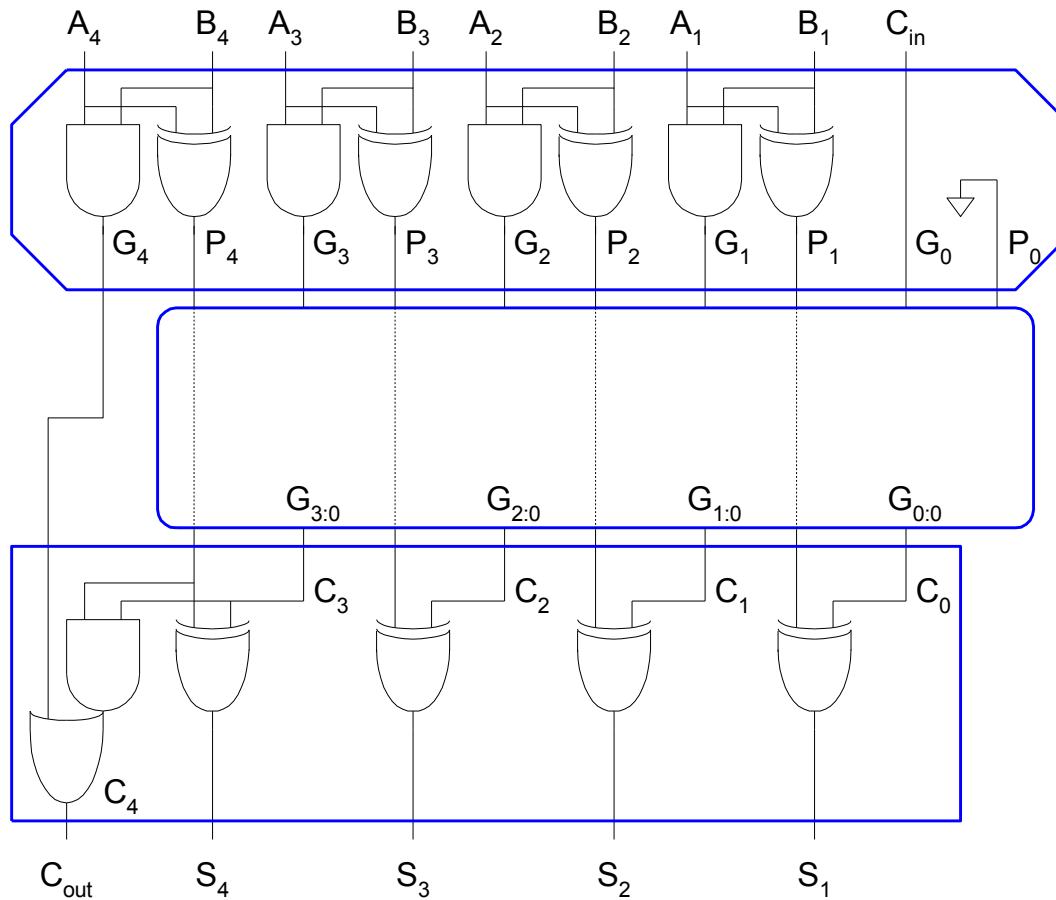

$$G_{0:0} \equiv G_0 = C_{in}$$

$$P_{0:0} \equiv P_0 = 0$$

1: Bitwise PG logic

$$G_{i:i} \equiv G_i = A_i \text{ g } B_i$$

$$P_{i:i} \equiv P_i = A_i \oplus B_i$$

2: Group PG logic

$$G_{i:j} = G_{i:k} + P_{i:k} \text{ g } G_{k-1:j}$$


$$P_{i:j} = P_{i:k} \text{ g } P_{k-1:j}$$

3: Sum logic

$$S_i = P_i \oplus G_{i-1:0}$$


Carry-Ripple Revisited
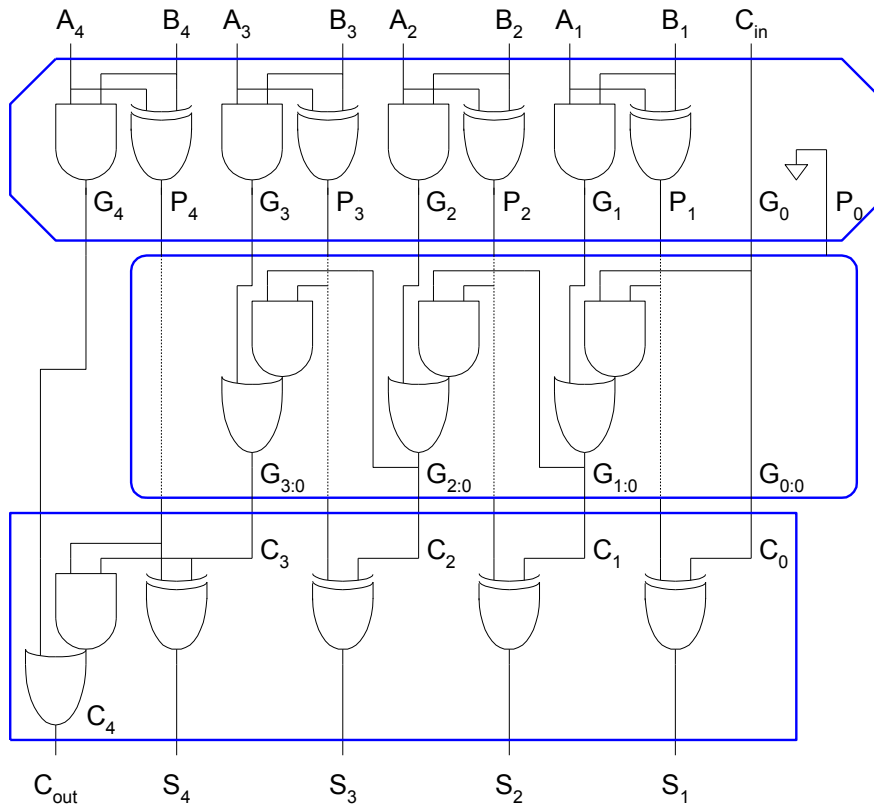
$$G_{i:0} = G_i + P_i \text{ g } G_{i-1:0}$$




Carry-Ripple PG Diagram
 
$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{\text{xor}}$$




PG Diagram Notation





Black cell

 


Gray cell

 

Buffer

    

Higher-Valency Cells

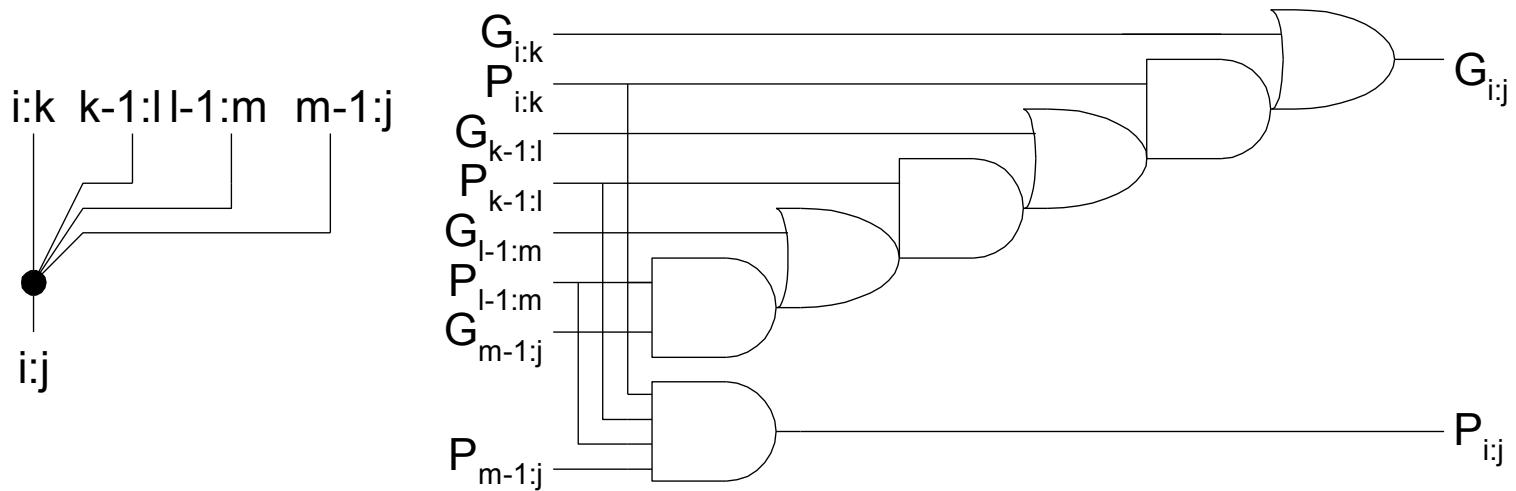




Manchester Carry Chain

$$C_0 = G_{0:0} = C_0$$

$$C_1 = G_{1:0} = G_1 + P_1 C_0$$

$$C_2 = G_{2:0} = G_2 + P_2 (G_1 + P_1 C_0)$$
 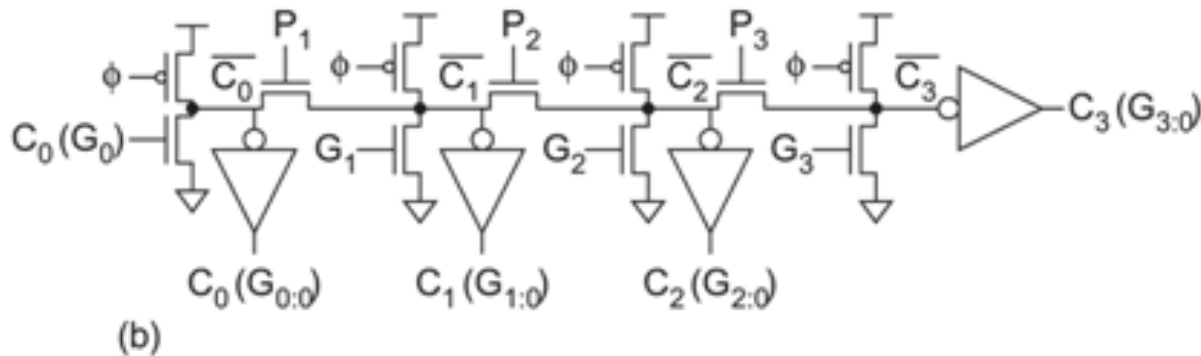 
$$C_3 = G_{3:0} = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 C_0))$$



Manchester Carry Chain

