
EE213

Digital Integrated Circuits II

Lecture 08A: Adders


Prof. Pingqiang Zhou

<http://sist.shanghaitech.edu.cn/faculty/zhoupq/Teaching/Spr17/Digital-IC-2.html>


ShanghaiTech University
School of Information Science and Technology

Materials Were Partly Taken From

- ❑ EE141: Digital Integrated Circuits, Spring 2010.
http://bwrccs.eecs.berkeley.edu/Courses/icdesign/ee141_s10/index.htm

 


Chapter 11

 


Chapter 10

Review: MIPS Processor

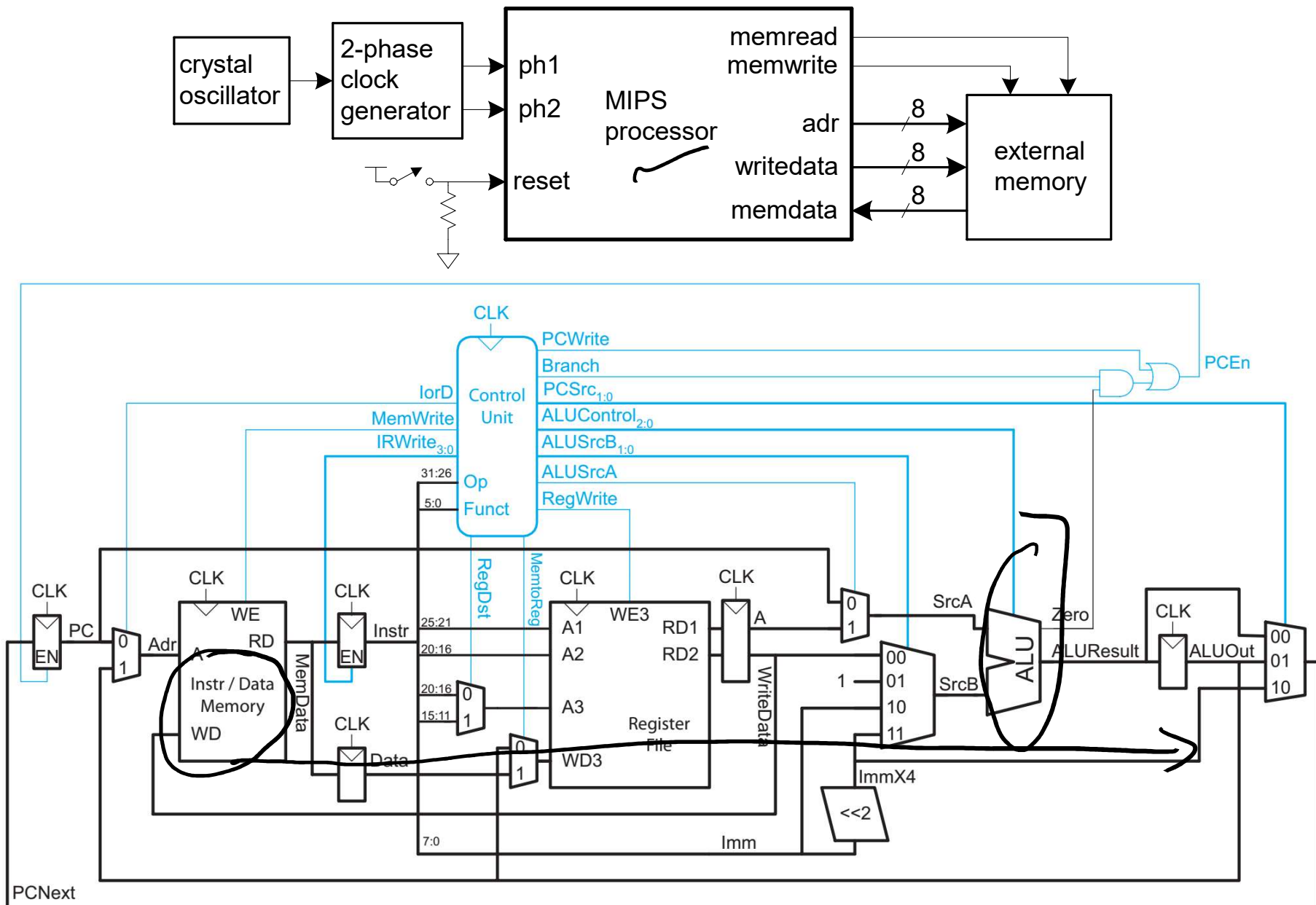

A Generic Digital Processor

 

□ Datapath

- Execution units
 - Adder, multiplier, divider, shifter, etc.
- Register file and pipeline registers
- Multiplexers, decoders

□ Control

- Finite state machines (PLA, ROM, random logic)


□ Interconnect

- Switches, arbiters, buses

□ Memory


- Caches (SRAMs), TLBs, DRAMs, buffers

An Intel Microprocessor - Itanium

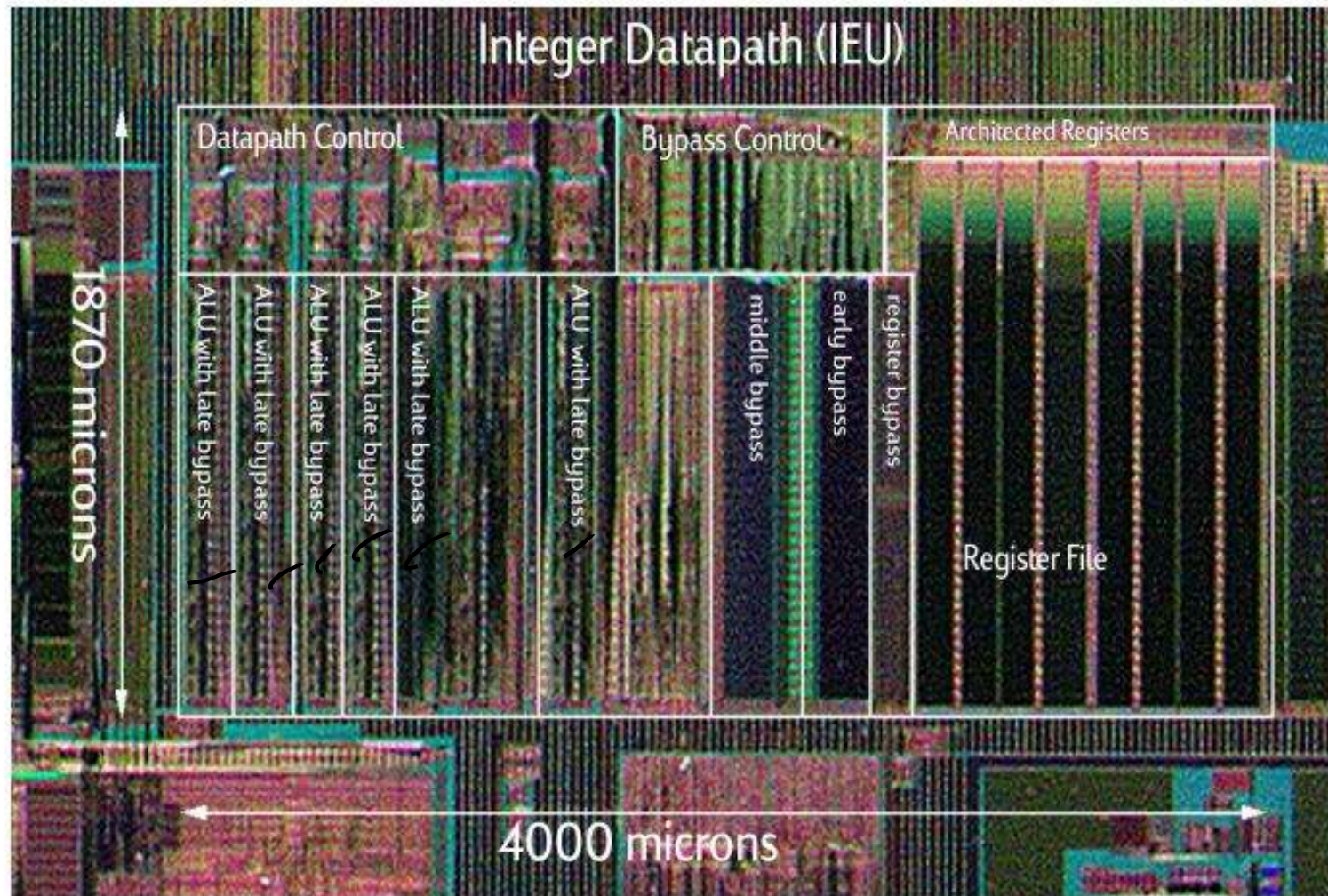

Fetzer, Orton, ISSCC'02

Itanium Integer Datapath (ALU)

 


Itanium has 6 integer execution units like this.

Bit-Sliced Datapath

From register files / Cache / Bypass

$A[0, 31]$
 $B[0, 32]$

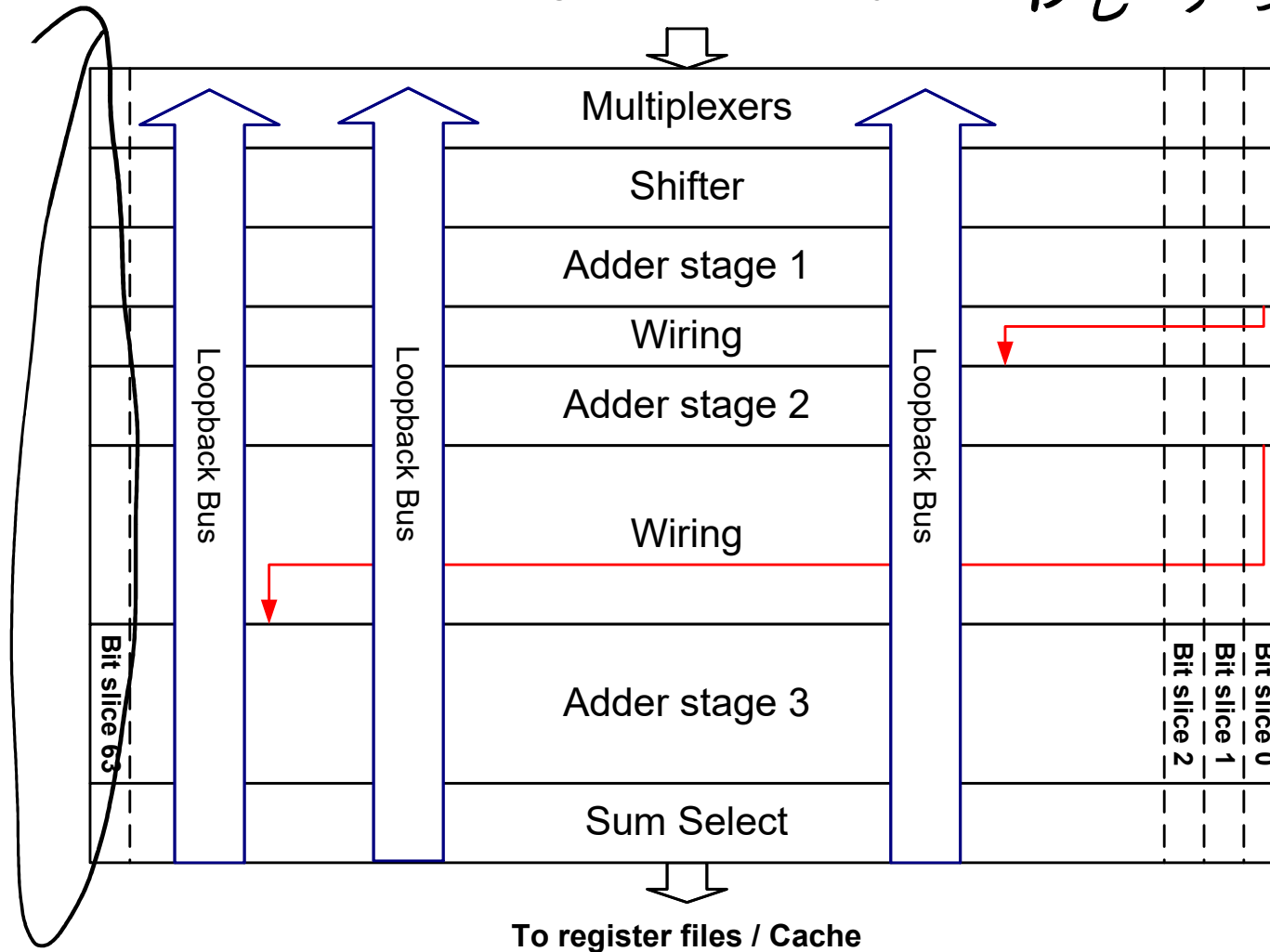


To register files / Cache

Outline

- ❑ Single-bit addition
- ❑ Circuit design considerations
 - Static CMOS adder
 - Mirror adder
 - Inversion property
 - Manchester Carry Chain
- ❑ Logic design considerations
 - Carry-bypass (or skip) adder
 - Carry-select adder
 - Tree Adder


(Single-Bit) Binary Addition

Half Adder

 

A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

Full Adder

 

A	B	C_{in}	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		