

Number system	Conversion	Logic Gates				Truth Table																					
Binary: 0/1 Decimal: 0~9 Hexadecimal: 0~F	B->D: add each '1's D->B: divide by 2 B<->H: 4bit B=1bit H	AND 	$x \cdot y$	NAND 	$\overline{x \cdot y}$	Show input sets and output sets in one table	<table><tr><td>x</td><td>y</td><td>f</td><td>$f = \overline{x}y$</td></tr><tr><td>0</td><td>0</td><td>0</td><td>$\overline{\overline{0}}0$</td></tr><tr><td>0</td><td>1</td><td>1</td><td>$\overline{0}1$</td></tr><tr><td>1</td><td>0</td><td>0</td><td>$1\overline{0}$</td></tr><tr><td>1</td><td>1</td><td>1</td><td>$1\overline{\overline{0}}$</td></tr></table> $f = x \oplus y$ (XOR)	x	y	f	$f = \overline{x}y$	0	0	0	$\overline{\overline{0}}0$	0	1	1	$\overline{0}1$	1	0	0	$1\overline{0}$	1	1	1	$1\overline{\overline{0}}$
x	y	f	$f = \overline{x}y$																								
0	0	0	$\overline{\overline{0}}0$																								
0	1	1	$\overline{0}1$																								
1	0	0	$1\overline{0}$																								
1	1	1	$1\overline{\overline{0}}$																								
OR 	$x + y$	NOR 	$\overline{x + y}$	XOR 	$x \oplus y$																						
NOT 	\overline{x}	XOR 	$x \oplus y$																								
Significant bit	Axioms and Rules for Boolean Algebra				BoolAlg Order	Sum of products																					
	$0 \cdot 0 = 0, 1 \cdot 1 = 1$ $0 \cdot 1 = 1 \cdot 0 = 0$ $x + 0 = x, \overline{x} = 1$ $x \cdot 0 = 0$ $x \cdot 1 = x$	$x \cdot x = x$ $x + \overline{x} = 1$ $\overline{\overline{x}} = x$ $x \cdot y = y \cdot x$ $x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x \cdot (y + z) = x \cdot y + x \cdot z$ $x + x \cdot y = x$ $xy + x\overline{y} = x$ $\overline{xy} = \overline{x} + \overline{y}$ $x + (\overline{x} \cdot y) = x + y$	Parenteses (bracket) → NOT → AND → OR	Add all midterms where output=1 $f = \sum m_{(f=1)}$ (Canonical term)																						
Product of sums	Synthesis and Cost	Multiplex (MUX)	2:1 Multiplex	 $f = A\overline{S} + BS$	 f_0 f_1 S_0 S_1																						
Add all maxterms where output=0 $f = \prod M_{(f=0)}$ (Canonical Term)	Synthesis: add all min/maxterms into minimal cost form Cost = #Gates + #inputs	Selects one signal between multiple signals Depends on another digital signal(s) "S"																									
module name (a,b,t,f) input a, b, t; output f; assign f=(~t&a) (t&b); endmodule	Hierarchy	Common cathode	Lookup table (LUT)	 x_0 x_1 f_0 f_1 f_2 f_3	Half Adder																						
	Add sub-modules into main module (similar with functions)	Turns on when segment value is 1 (anode -> 0)	Programmable gate array, hold interconnection 'code' of the gates		 a b S_1 S_0 1 <																						